



Introduction to FPGAs

Chun-Jen Tsai and Lan-Da Van
Department of Computer Science
National Yang Ming Chiao Tung University
Taiwan, R.O.C.
Fall, 2025




History of the FPGAs

Mat 3

- ◆ Before the invention of Field Programmable Gate Array (FPGA), there are many different programmable IC such as PLA, PAL, CPLD, etc.
 - These programmable IC's have very limited logic capacity.
 - CPLD IC's are still popular in industry because their “digital logic programs” do not disappear when the power is off.

- ◆ R. H. Freeman invented the first practical FPGA in 1985[†].
 - Freeman and Vonderschmitt co-funded Xilinx in 1984.
 - Xilinx is the first fabless IC design house in the world.
 - TSMC enters the IC OEM business for fabless IC design houses in 1987.

 [†] R. H. Freeman, “Configurable Electrical Circuit Having Configurable Logic Elements and Configurable Interconnect,”
US Patent 4,870,302, Sep. 26, 1989







Combinational PLDs

Mat 3

 
- ◆ Programmable two-level logic
 - an AND array and an OR array



(a) Programmable read-only memory (PROM)

 

(c) Programmable logic array (PLA)

 

(b) Programmable array logic (PAL)



 


 

Diagram of 32x8 ROM

Mat 3

 
- programmable interconnections
 - ◆ close (two lines are connected)
 - ◆ or open
 - ◆ A fuse that can be blown by applying a high voltage pulse






PLA Example

Mat 3

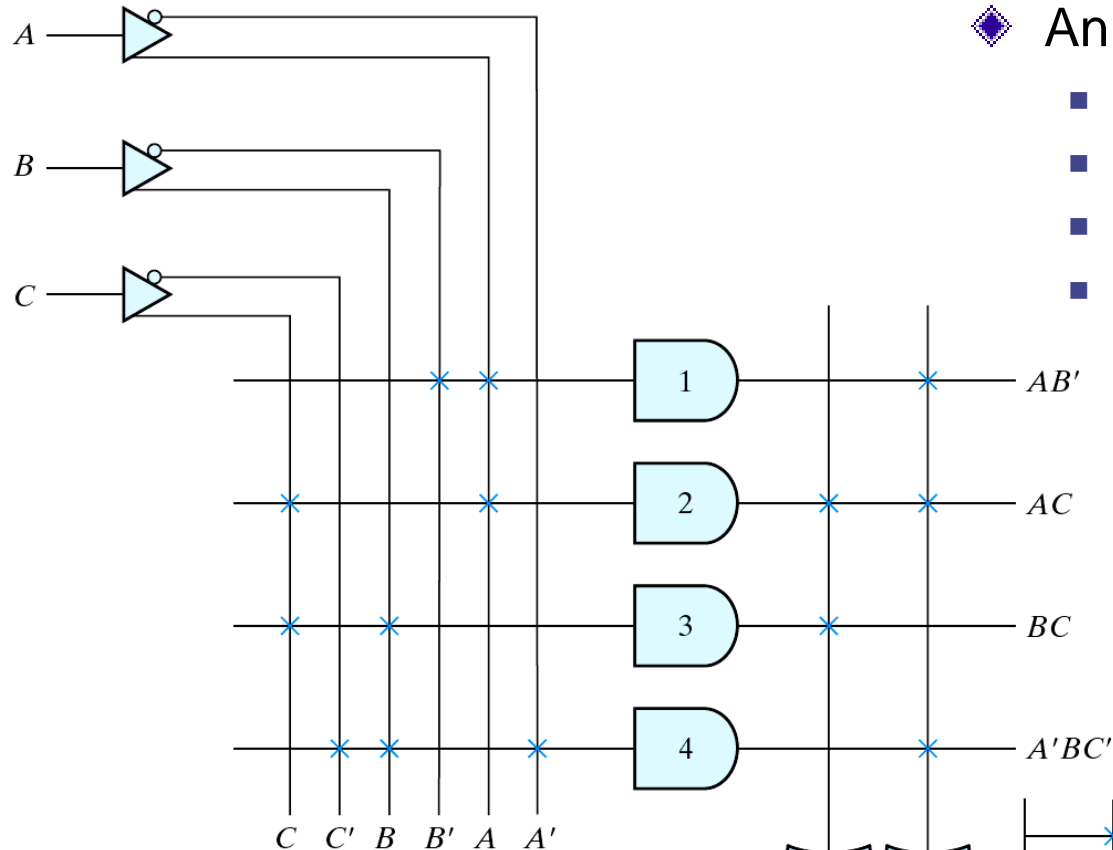

- ◆ An example
- $F1 = AB' + AC + A'BC'$
 - $F2 = (AC + BC)'$
 - XOR gates
 - can invert the outputs

 PLA with three inputs, four product terms, and two outputs







PAL Example

$$w = ABC' + A'B'CD'$$

$$x = A + BCD$$

$$y = A'B + CD + B'D'$$

$$z = w + AC'D' + A'B'C'D$$

 
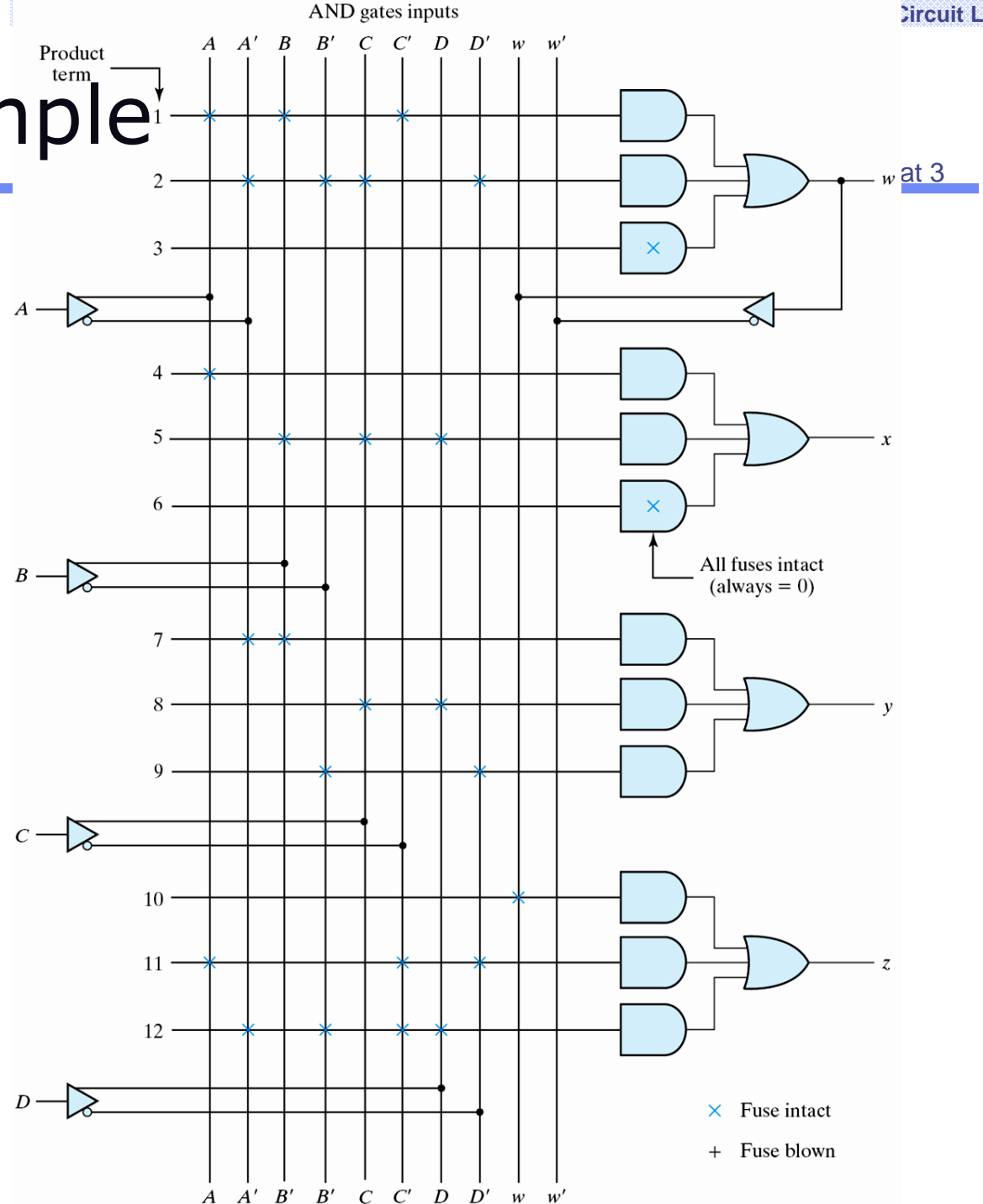




Programming Concept of the FPGA

Mat 3

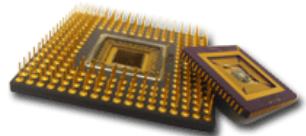 - ◆ Theoretically speaking, creating a digital logic on an FPGA strictly follows the “stored program concept” of software programming.
 - Thus, FPGA coding should be regarded as “software coding”.
- ◆ Stored program concept:
The computing behavior of a piece of hardware is controlled by information stored in memory devices.





Digital Circuits in an FPGA

Mat 3

- ◆ The basic ideas of FPGA's is to inter-connect small “truth tables” to emulate complex digital circuits.
 - In an FPGA, these tables are called “Lookup Table” (LUT).

Table 1

input	output
0000	1
0001	0
...	...
1111	1

...


Table 4

input	output
0000	0
0001	1
...	...
1111	1

Table 5

input	output
0000	0
0001	0
...	...
1111	1

 Each table is equivalent to a n-to-1 gate, where n = 4 or 6 for Xilinx FPGA's.







Programmability of the FPGA

Mat 3

- ◆ FPGA still adopts the “stored program concept”.
 - Both **the n-to-1 gates** and **the wires** can be programmed.

 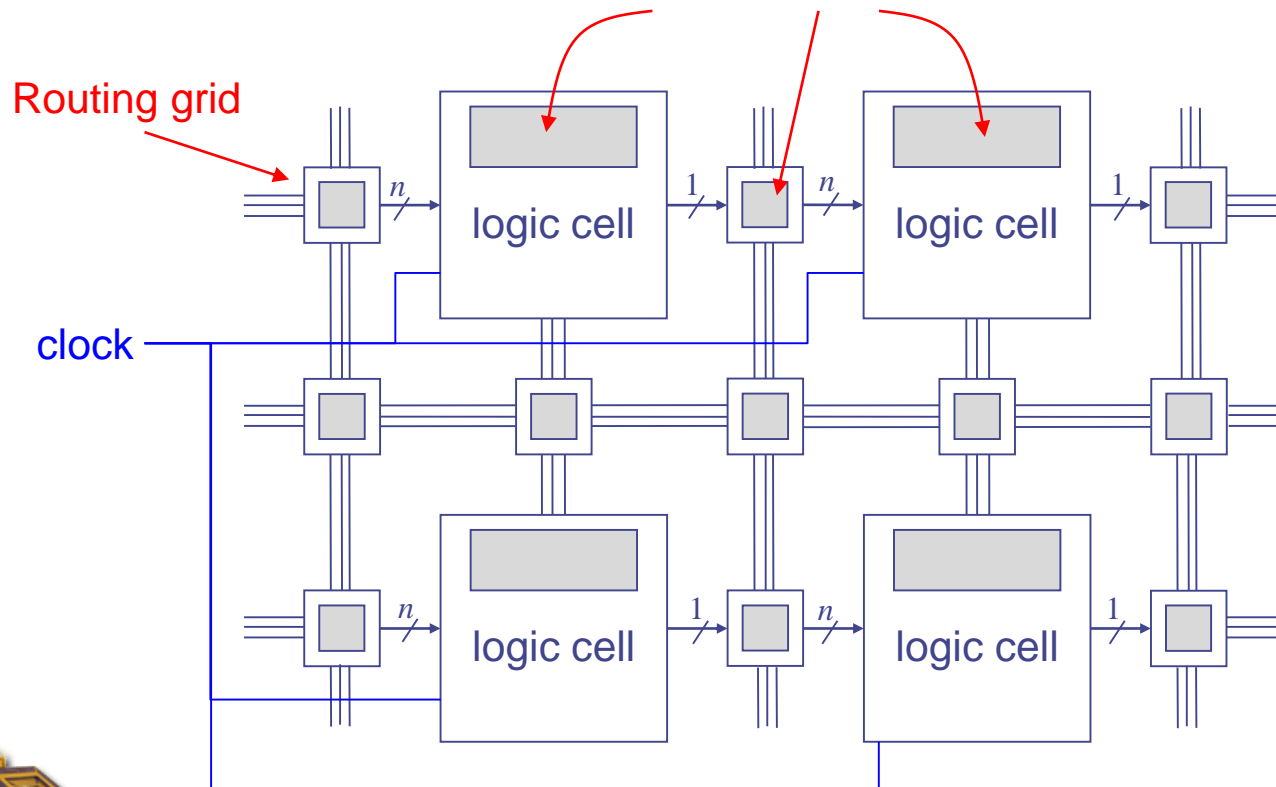FPGA programs are stored in distributed memory bits







A Generic Logic Cell

Mat 3

◆ Basic logic cell (LC) structure:

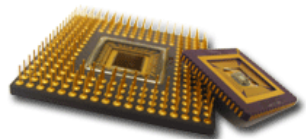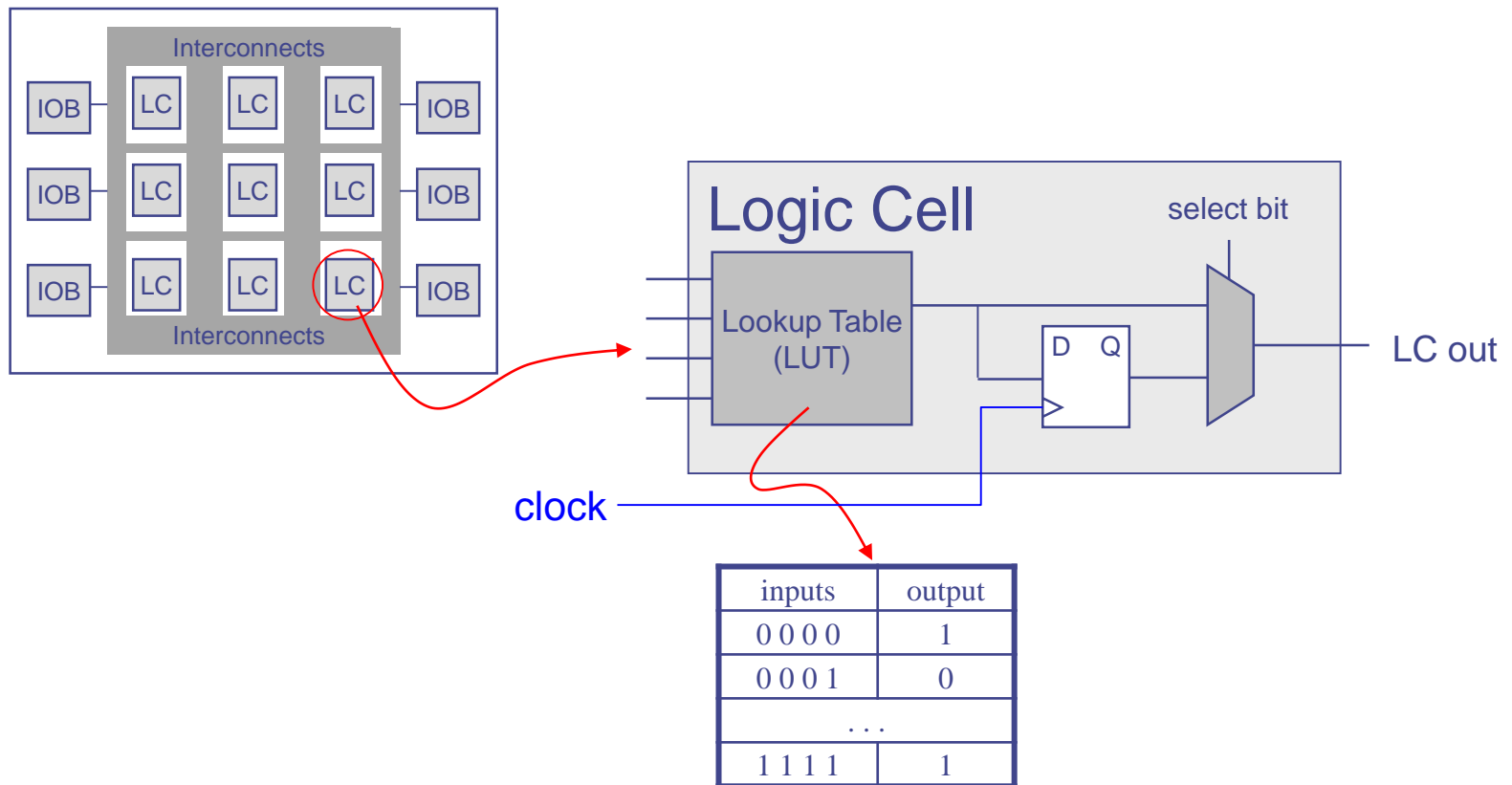




Features of SRAM-based LUT

Mat 3

- ◆ SRAM is often used to implement LUT, the properties of this type of LUT is as follows:
 - An n -bit input LUT can handle function of 2^n different inputs.
 - All logic functions take the same amount of area.
 - All functions have the same delay.
 - ◆ For CMOS custom logics, XOR is much slower than NAND.
 - Burn power even at idle
- ◆ An LUT is more “powerful” than a two-input gate.
 - Gate-count is not a good measure of FPGA logic cost.
 - For a static gate, an n input NAND/NOR gate has $\sim 2n$ transistors.
 - For an FPGA LC, 4-input LUT has 128 transistors in SRAM, 96 in multiplexer.

 




Function Implementation with LUTs

Mat 3


- ◆ The datapath that implements $F = A'B'C + A'BC' + AB$ is as follows, the LUT4 has entries as follows:

$X_1 X_2 X_3 X_4$	F
0000	0
0001	0
0010	1
0011	1
...	...
1111	1

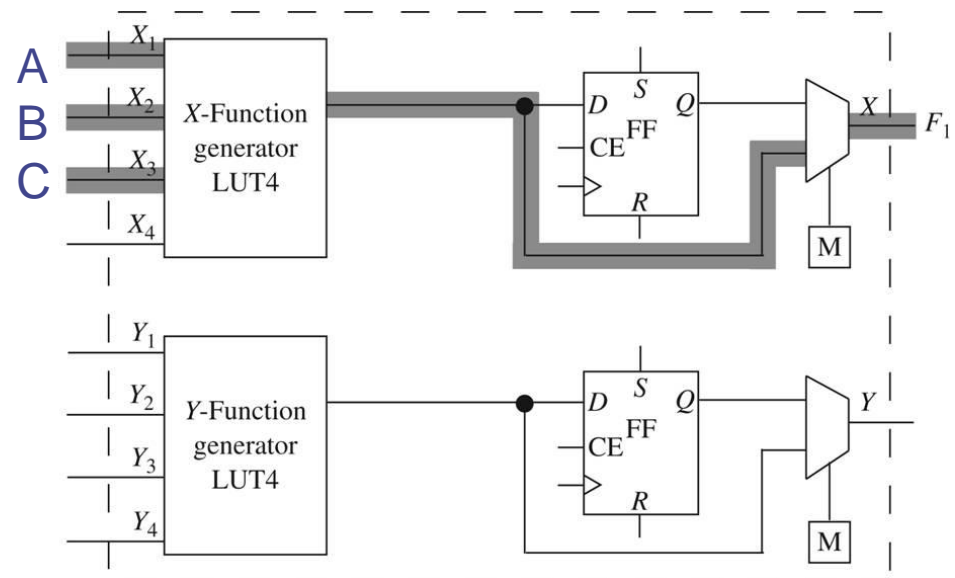LUT4 table entries
(red means don't care)



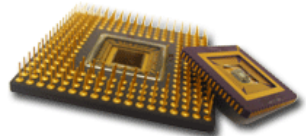- ◆ A function with more than 4 variables can always be decomposed to the sum (OR) of 4-variable function.







Carry Chains in FPGA

Mat 3

 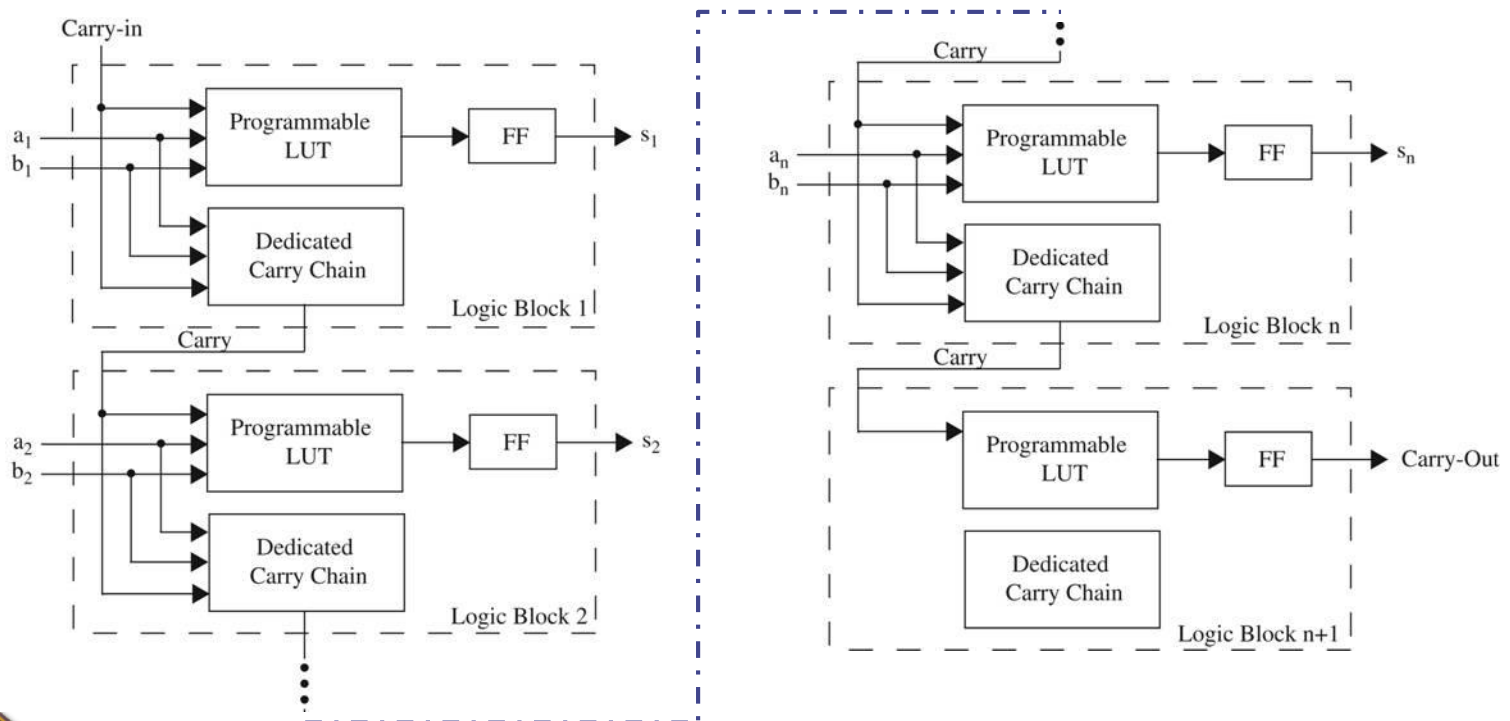- ◆ Since additions are very important, many FPGAs have dedicated circuits for carry calculation and propagation.
 - Both carry look-ahead and carry-ripple adders can be implemented efficiently on FPGAs.






Review: Look-ahead Carry Generator

Mat 3

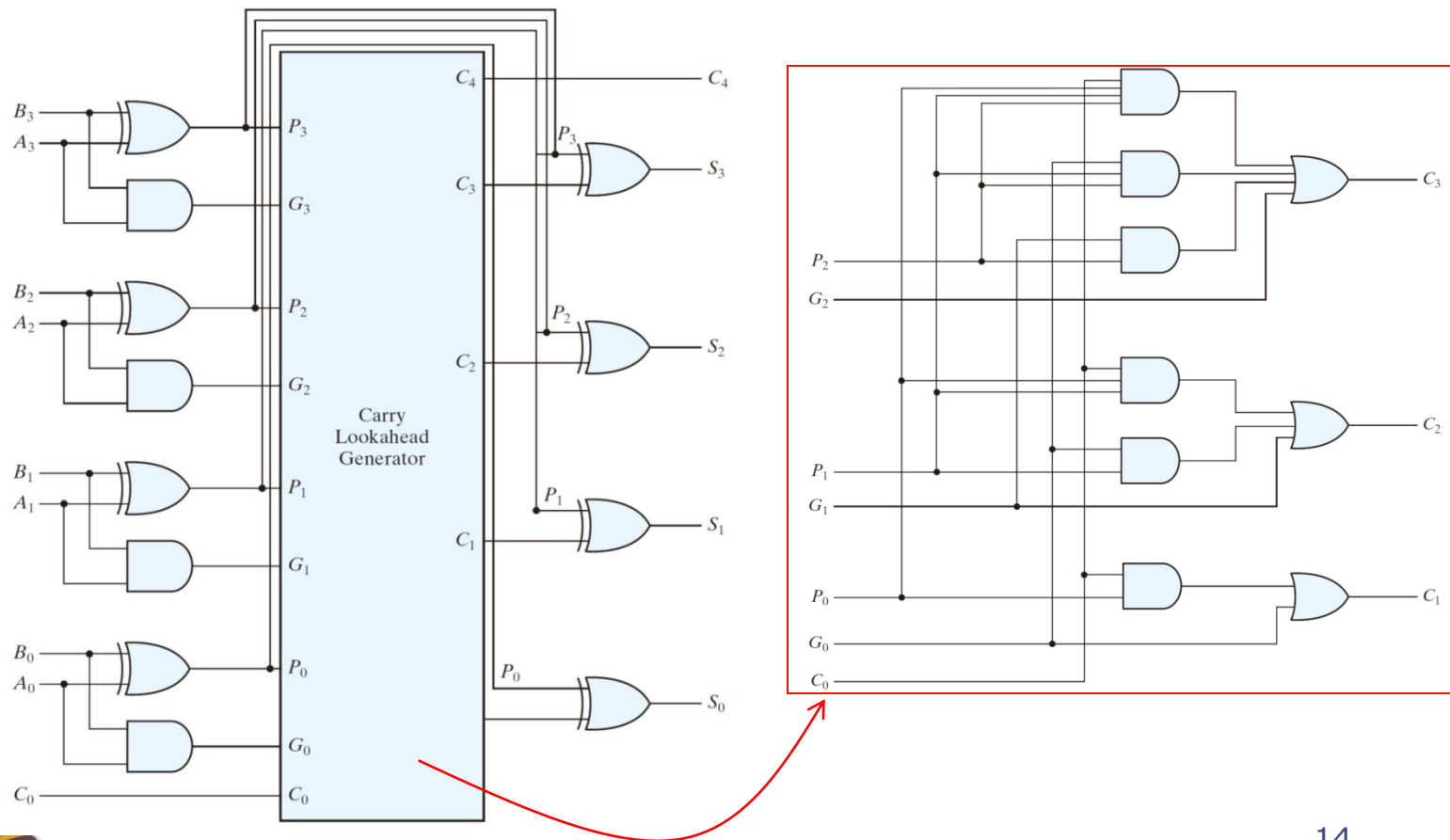
- ◆ A look-ahead carry adder is more efficient than a carry-ripple adder:






Review: Look-ahead Carry Generator


Mat 3

 

CLA GEN

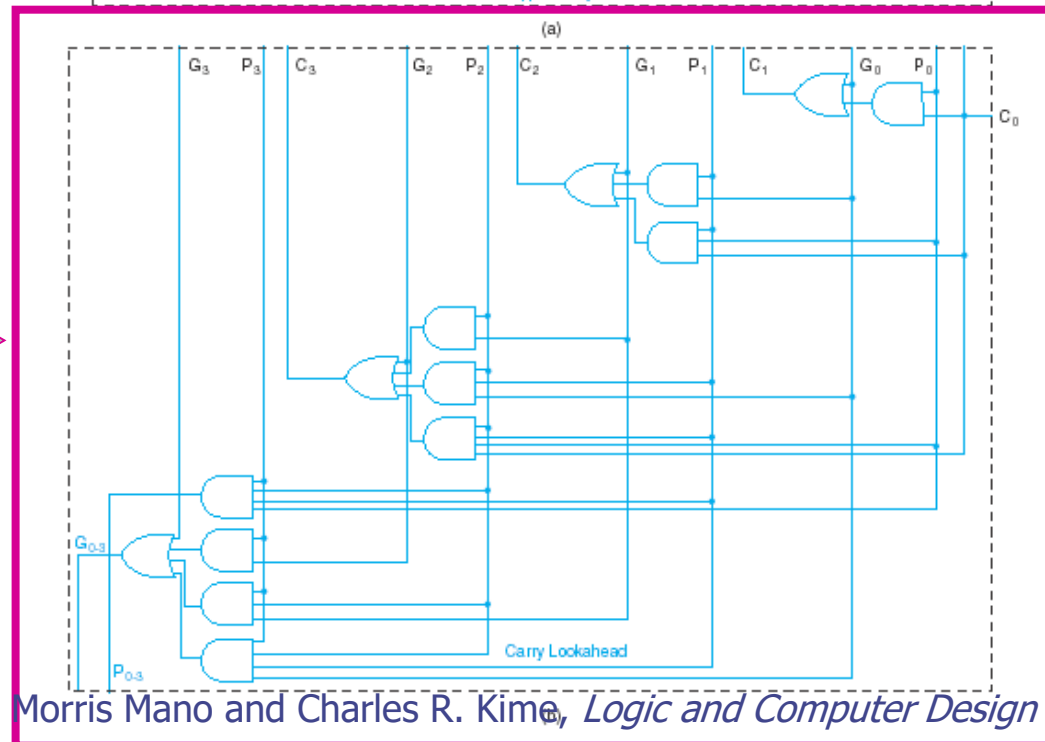

 Source: M. Morris Mano and Charles R. Kime, *Logic and Computer Design Fundamentals*.






Programmable Interconnect Points



Mat 3

- ◆ The routing wire in an FPGA is programmed using a single-bit SRAM cell connected to a transistor:

Connect/disconnect a single wire:

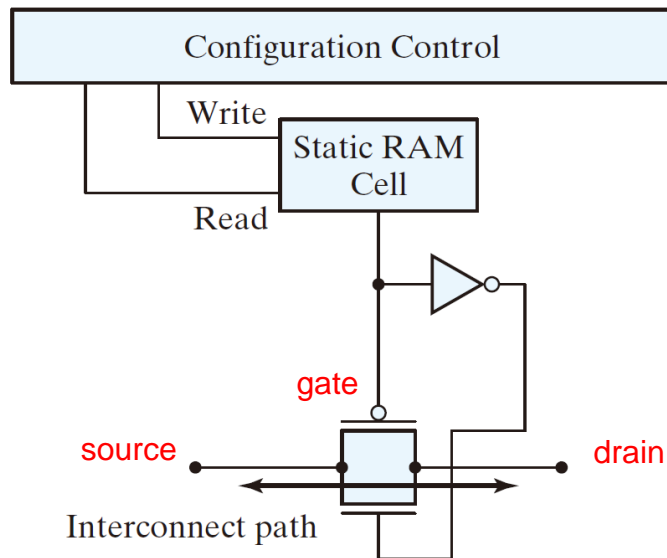

Routing a signal:


 
 




Interconnect Architecture

Mat 3

   - ◆ On an FPGA, we must be able to control
 - Connections from wiring channels to LCs
 - Connections between wires in the wiring channels







Place and Route Problem

Mat 3

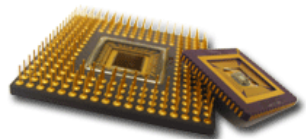 - ◆ Wiring among LCs are organized into channels.
 - Channels are arranged horizontally and vertically on the chip.
 - There are many wires per channel.
- ◆ Connections between wires made at programmable interconnection points
- ◆ An EDA tool must choose:
 - Channels from source to destination
 - Wires within the channels






Xilinx FPGA Family

Mat 3

- ◆ The Xilinx FPGA generations are coupled with the TSMC manufacturing process.
 - Usually two lines of product before the TSMC 28nm process
- ◆ Old products before the 28 nm TSMC process
 - Virtex-II / Spartan-2 (130 nm)
 - Virtex-4 / Spartan-3 (90nm) } 4-input LUT
 - Virtex-5 (65 nm)
 - Virtex-6 (40 nm)/ Spartan-6 (45 nm) } 6-input LUT
- ◆ New products after the 28 nm TSMC process
 - Virtex-7 / Kintex-7 / Artix-7 / Zynq-7 (28 nm)
 - Virtex UltraScale / Kintex UltraScale (20nm)
 - Virtex UltraScale+ / Zynq UltraScale+ (16 nm FinFET+) } 6-input LUT

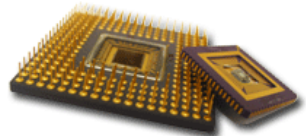






Xilinx FPGA Architecture

Mat 3

- ◆ Xilinx FPGAs are composed of CLBs, BRAMs, Multipliers (in DSP slices), CMTs, and IOBs.

XC7A35T:

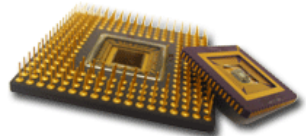  - 2,600 CLBs
- 1800 Kb BRAMs
- 90 25x18-bit multipliers
- 5 CMTs







CLB Architecture of Artix-7

Mat 3

  - ◆ The CLB architecture of an Artix-7 FPGA:
- The main resources for logic synthesis
 - Each CLB contains two slices, each slice four logic cells.
 - Each CLB is connected to a switch matrix.
 - Carry chain runs vertically in a column from one slice to the one above.







CLB Architecture of Spartan II

Mat 3

 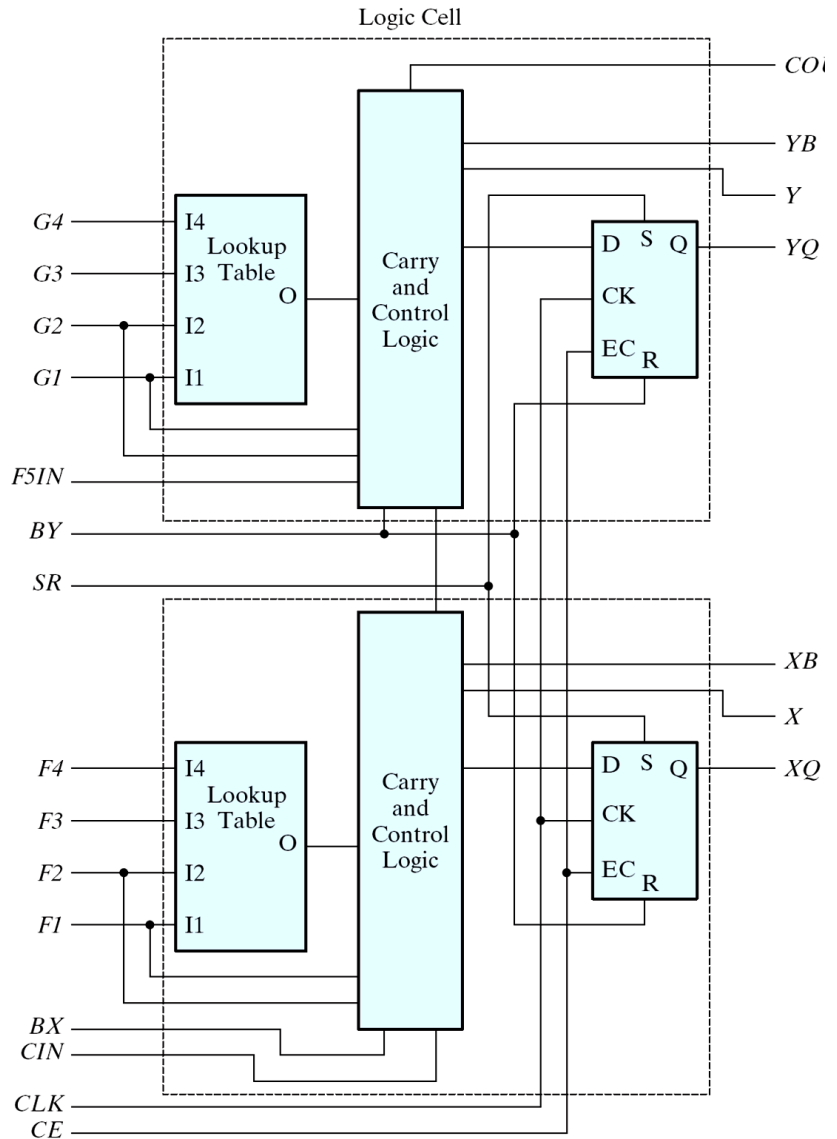- Each CLB contains four logic cells, organized as a pair of slices.
- Each slice has a four-input lookup table, logic for carry and control, and a D-type flip-flop.
- Spartan II family provides the flexibility and capacity of an on-chip block RAM.
- 1 CLB = 2 slices = 4 logic cells






Slice Structure


Mat 3

- ◆ The left-hand and right-hand slices have different architecture:


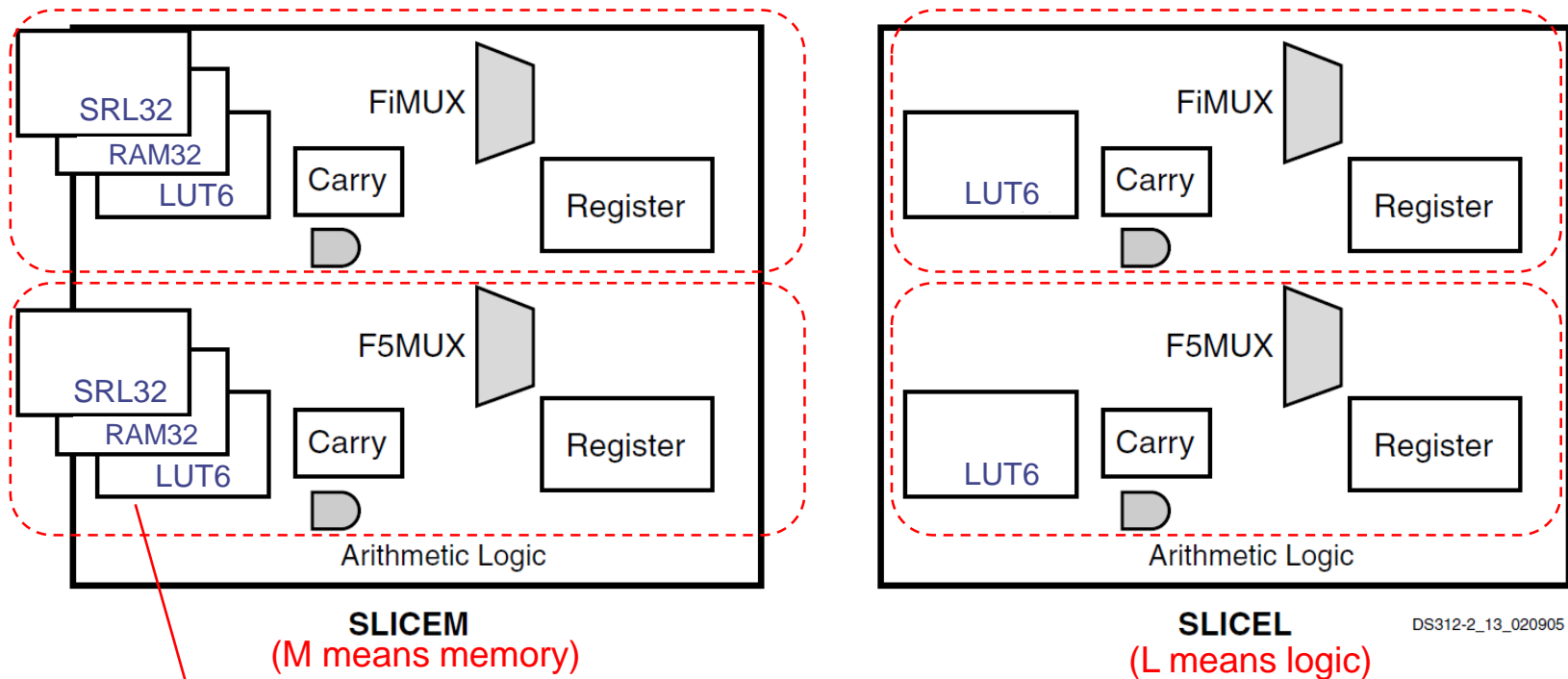


DS312-2_13_020905

LUT6 can be used as a shift-register or a small RAM block, i.e., a distributed RAM

 

Mat 3

 
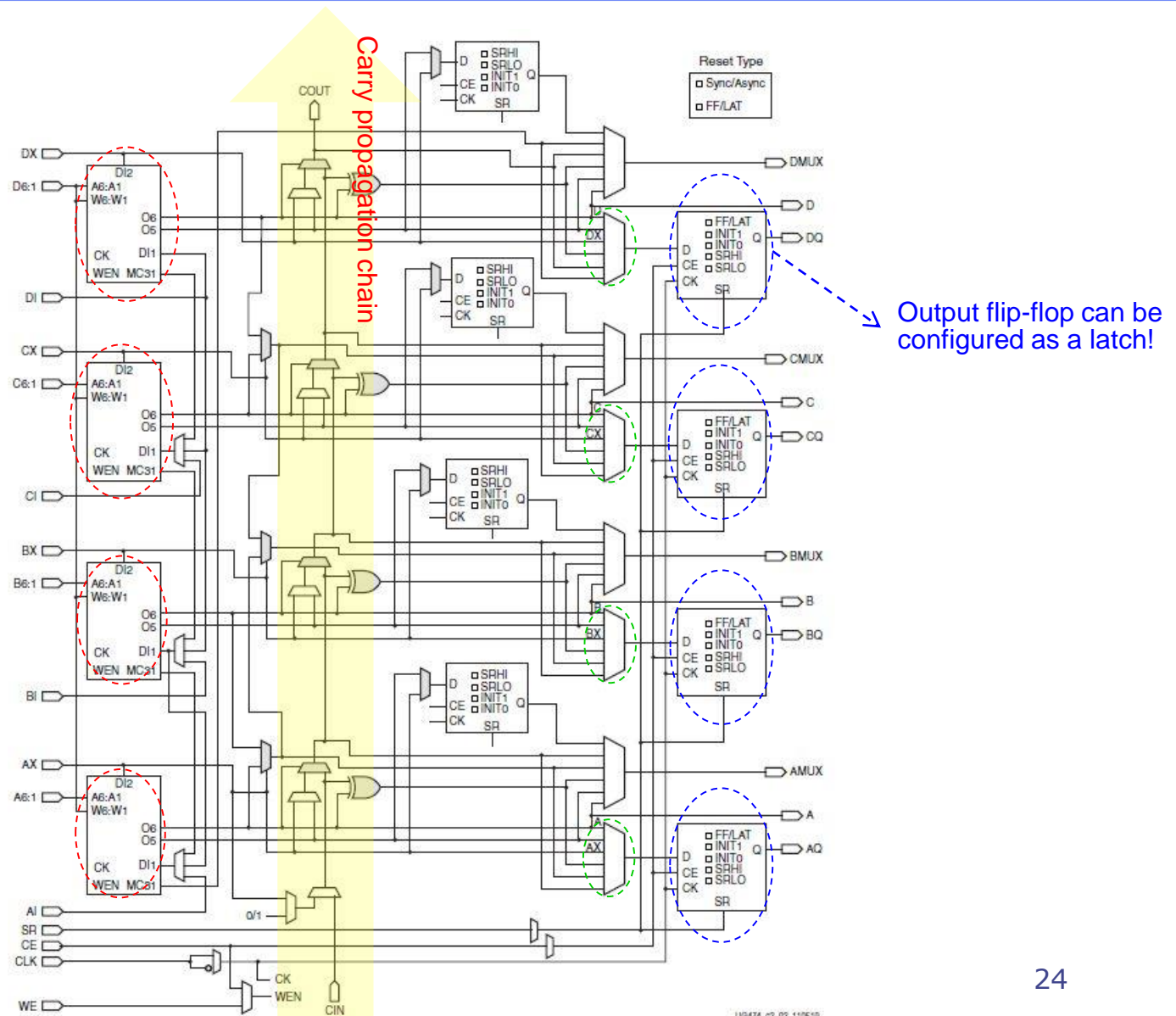




Synthesis of a Large Multiplexor

Mat 3

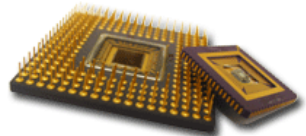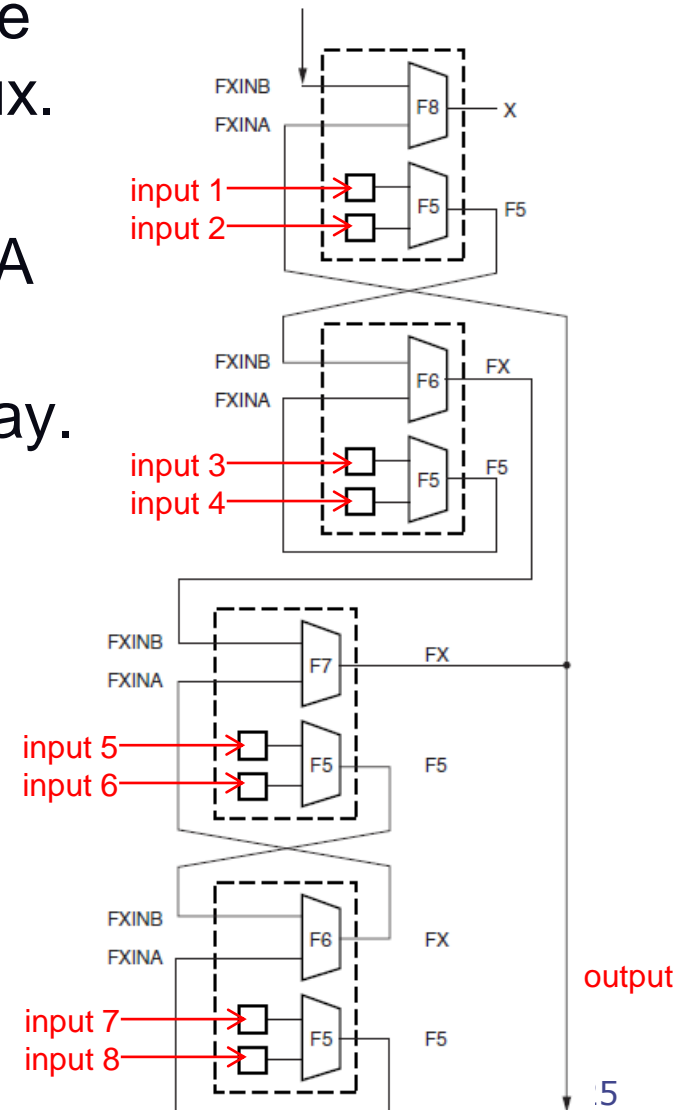- ◆ Several 2-to-1 MUXes can be combined to form a large mux.
- ◆ A large mux consumes FPGA resources significantly and creating long signal path delay.
 - Please use them wisely.







Configurable LUT6 or LUT5

Mat 3

 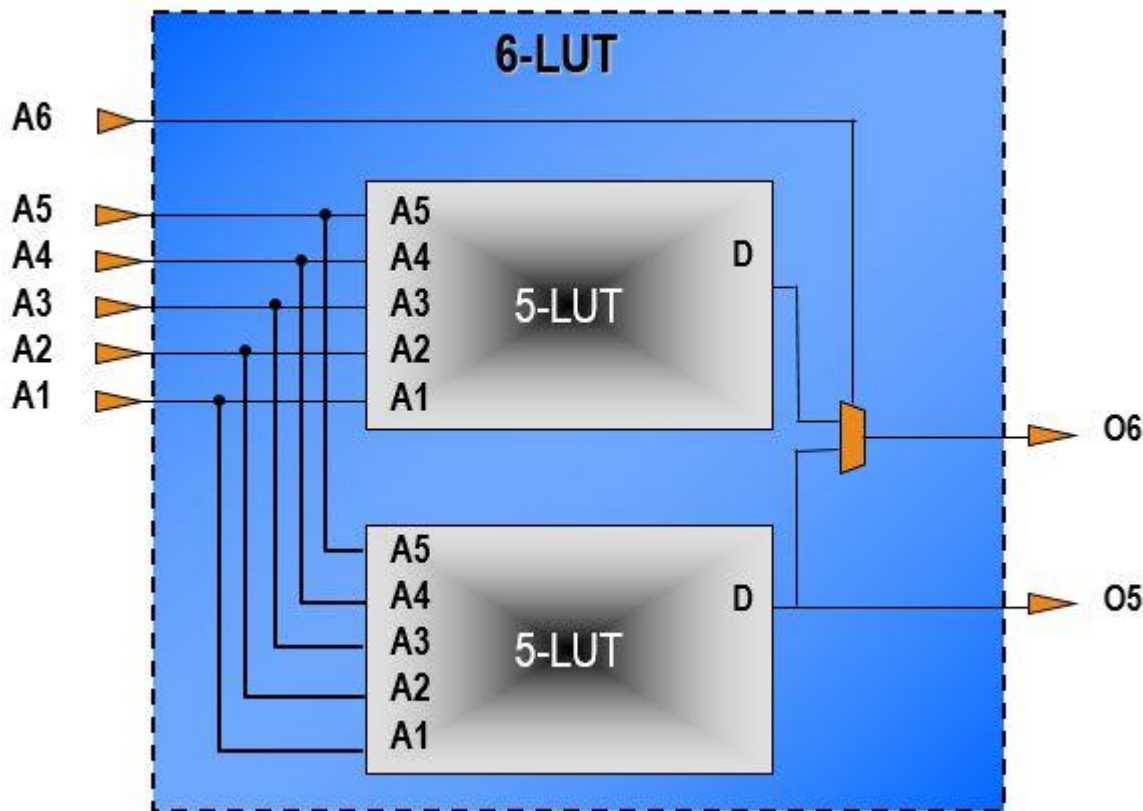- ◆ Each 6-input LUT can also be configured as two 5-input LUT's for logic synthesis:







Multi-Purpose LUT in SliceM

Mat 3

  - ◆ The LUTs in SliceM can also be configured as either 32-bit shift registers or 32-bit RAM blocks (called distributed RAM).





LUT as a Distributed RAM

Mat 3




◆ LUT can be used as a distributed RAM.

- Each unit is a 32×1 RAM, where 5 of the LUT input lines becomes the address lines of a RAM block.
- LUTs can be cascaded to increase RAM size.
- Each LUTs can be used to Implement either
 - ◆ a 64×1 -bit RAM
 - ◆ a 32×2 -bit RAM
 - ◆ a 32×1 -bit RAM with dual output ports

◆ Synchronous write

◆ Synchronous / Asynchronous read

   - Output flip-flop is used for synchronous read.







LUT as a Shift Register

Mat 3

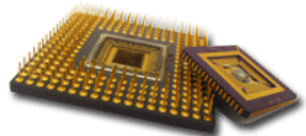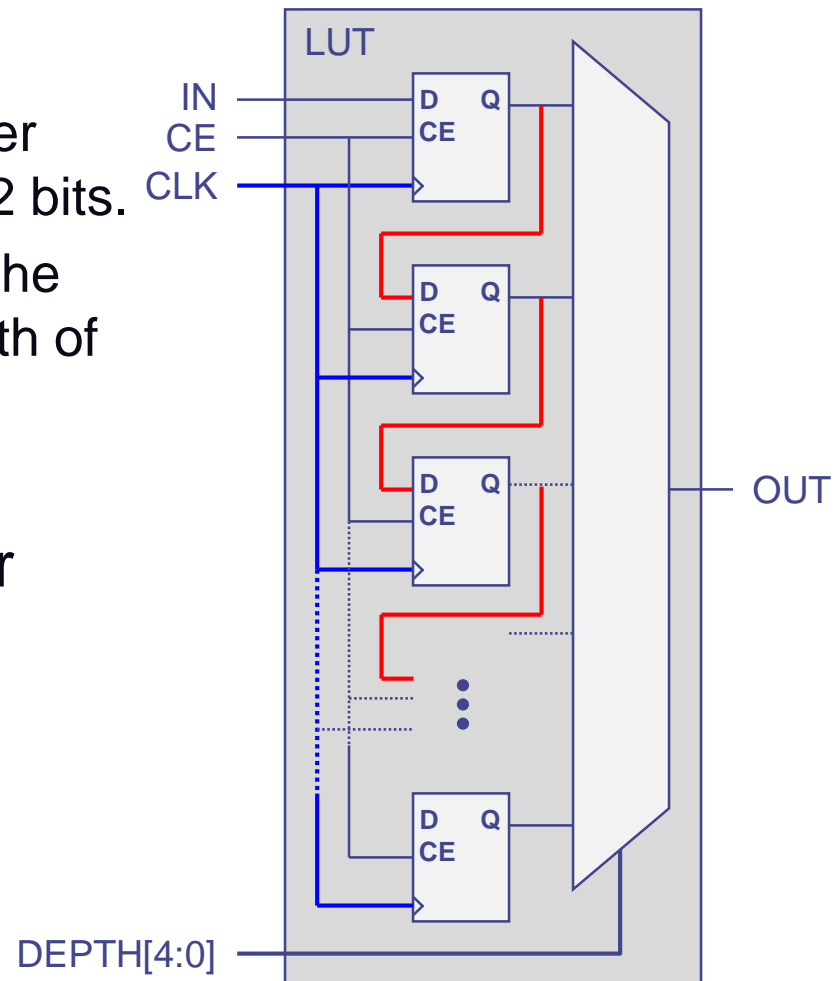- ◆ Each LUT can be configured as a shift register.
 - Bit depth of the shift register is configurable from 1 to 32 bits.
 - The 5 of the input lines of the LUT is used to set the depth of the shift register.
- ◆ Multiple LUTs can be cascaded to form a larger shift register.






DSP Slice

Mat 3

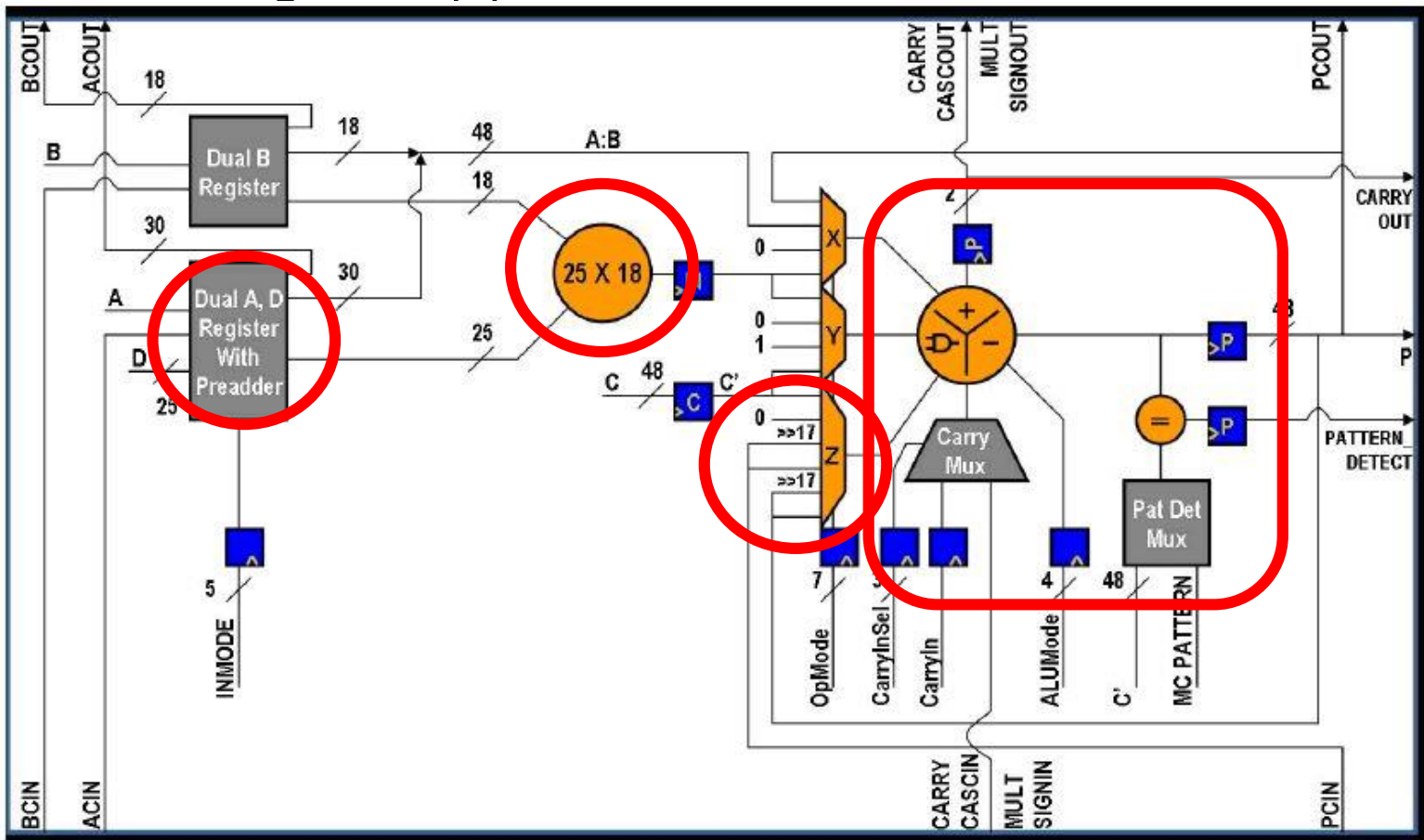- ◆ Each DSP slice contains:
 - 25x18 multiplier, 25-bit pre-adder, 48-bit ALU, 17-bit shifter
 - Configurable pipeline






Configuring SRAM-based FPGA

Mat 3

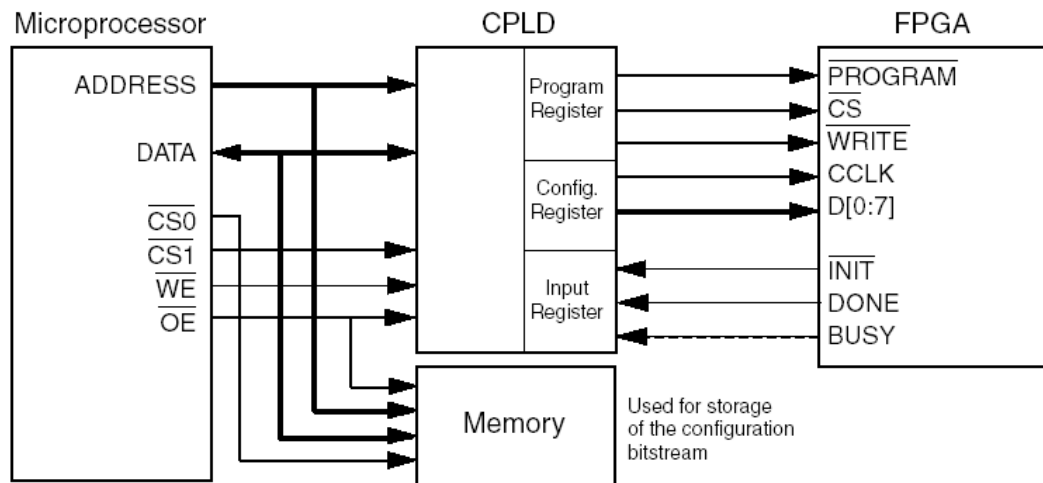- ◆ There are several ways to configure an FPGA.
 - A host PC configures FPGA using JTAG interface, not good for “turn-key” systems.
 - FPGA boots in master mode, reads configuration data from a flash ROM (or SD card) through the SPI bus.
 - FPGA boots in slave mode, a microcontroller (through GPIO) or a CPLD can be used to configure an FPGA.




X502_16_111507



Behavior of FPGA Configuration


Mat 3

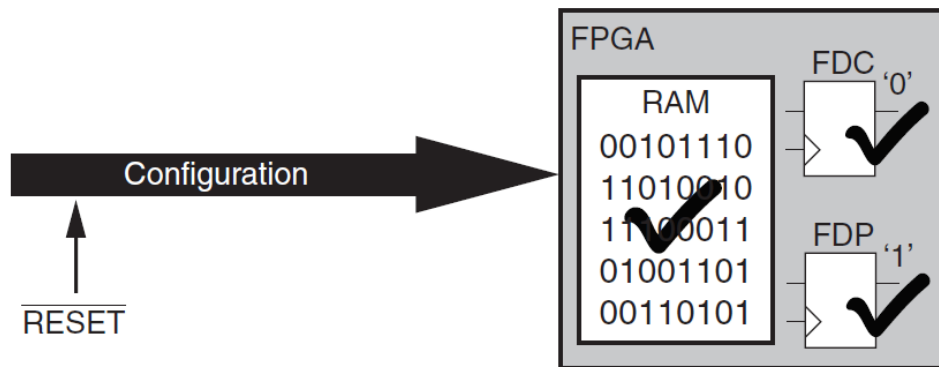- ◆ When a Xilinx FPGA is configured or reconfigured, every cells are initialized.
 - Configuration has the same effect as a global reset and it sets/presets all the flip-flops and initializes all RAM cells.



WP272_06_010708

 FDC – D Flip-flops with asynchronous clear
FDP – D Flip-flops with asynchronous preset





References

Mat 3

- ◆ Mentor Graphics, *The Design Warrior's Guide to FPGAs Devices, Tools, and Flows*, ISBN 0750676043, 2004.
- ◆ Xilinx, *7 Series FPGAs Configurable Logic Block User Guide*, Xilinx UG474, v1.8, Sep. 27, 2016.
- ◆ P. Garrault and B. Philofsky, *HDL Coding Practices to Accelerate Design Performance*, Xilinx WP231, Jan. 6, 2006.
- ◆ Xilinx, *Using Digital Clock Managers (DCMs) in Spartan-3 FPGAs*, XAPP462, Jan. 2006.
- ◆ M. Peattie, *Using a Microprocessor to Configure Xilinx FPGAs via Slave Serial or SelectMAP Mode*, Xilinx AN502, Aug. 2009.

